

# Agenda

- Announcement: Second Mini-test Wed 06.10 or Thu 7.10 at 15-17 in SM221

We discuss

- questions raised in previous Minute reports,
- some words about oscillator design,
- a recipe for scaling up in frequency,
  - example: Phase shifter scaled up to 18 MHz
- Video about oscilloscope probes.

Why does the oscillator's sinusoidal waveform wander in simulations but not in practice? Is that the fault of a simulation model that causes two resonant circuits, the waves of which interfere with each other and that effect is eliminated in the real world?

Oscillator is inherently a singular system (recall the oscillation condition where we divide by zero).

That makes it not easy for numerical simulations:

- I suppose that some of you noticed how slowly the simulation time increased compared to “real time”.
- Often a general solution method is not the best for singular systems.
- Notice also that it takes some time also for the real circuit before the transients vanish and steady state operation is achieved.

I actually presented my question on the Monday session, but I think the others might also be interested in the answer I received from Jari, and so I decided to ask it again, but this time publicly: What are the key differences between the use cases of 2N3904 and TSP10 transistors we have used so far and why?

See next slides

# Do we need two different transistors?

- We use KSP10 for
  - amplifier
  - oscillator
  - Modulator

**FAIRCHILD**  
SEMICONDUCTOR®

**KSP10**


VHF/UHF transistor

**NPN Epitaxial Silicon Transistor**

TO-92

1. Base 2. Emitter 3. Collector

KSP10

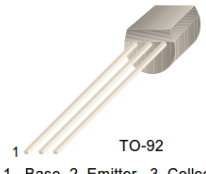

- We use 2N3709 for
  - audio amplifier

**ST**

**2N3904**

SMALL SIGNAL NPN TRANSISTOR

PRELIMINARY DATA

Ordering Code	Marking	Package / Shipment
2N3904	2N3904	TO-92 / Bulk
2N3904-AP	2N3904	TO-92 / Ammopack



- SILICON EPITAXIAL PLANAR NPN TRANSISTOR
- TO-92 PACKAGE SUITABLE FOR THROUGH-HOLE PCB ASSEMBLY
- THE PNP COMPLEMENTARY TYPE IS 2N3906

**APPLICATIONS**

- WELL SUITABLE FOR TV AND HOME APPLIANCE EQUIPMENT
- SMALL LOAD SWITCH TRANSISTOR WITH HIGH GAIN AND LOW SATURATION VOLTAGE

TO-92 Bulk

TO-92 Ammopack

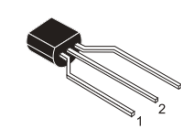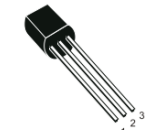

Symbol	Parameter	Test Conditions	Min.	Typ.	Max.	Unit
$I_{CEX}$	Collector Cut-off Current ( $V_{BE} = -3\text{ V}$ )	$V_{CE} = 30\text{ V}$			50	nA
$I_{BEX}$	Base Cut-off Current ( $V_{BE} = -3\text{ V}$ )	$V_{CE} = 30\text{ V}$			50	nA
$V_{(BR)CEO}^*$	Collector-Emitter Breakdown Voltage ( $I_B = 0$ )	$I_C = 1\text{ mA}$	40			V
$V_{(BR)CBO}$	Collector-Base Breakdown Voltage ( $I_E = 0$ )	$I_C = 10\text{ }\mu\text{A}$	60			V
$V_{(BR)EBO}$	Emitter-Base Breakdown Voltage ( $I_C = 0$ )	$I_E = 10\text{ }\mu\text{A}$	6			V
$V_{CE(sat)}^*$	Collector-Emitter Saturation Voltage	$I_C = 10\text{ mA}$ $I_C = 50\text{ mA}$ $I_B = 1\text{ mA}$ $I_B = 5\text{ mA}$			0.2 0.2	V V
$V_{BE(sat)}^*$	Base-Emitter Saturation Voltage	$I_C = 10\text{ mA}$ $I_C = 50\text{ mA}$ $I_B = 1\text{ mA}$ $I_B = 5\text{ mA}$	0.65		0.85 0.95	V V
$h_{FE}^*$	DC Current Gain	$I_C = 0.1\text{ mA}$ $I_C = 1\text{ mA}$ $I_C = 10\text{ mA}$ $I_C = 50\text{ mA}$ $I_C = 100\text{ mA}$ $V_{CE} = 1\text{ V}$ $V_{CE} = 1\text{ V}$ $V_{CE} = 1\text{ V}$ $V_{CE} = 1\text{ V}$ $V_{CE} = 1\text{ V}$	60 80 100 60 30		300	
$f_T$	Transition Frequency	$I_C = 10\text{ mA}$ $V_{CE} = 20\text{ V}$ $f = 100\text{ MHz}$	250	270		MHz
$C_{CBO}$	Collector-Base Capacitance	$I_E = 0$ $V_{CB} = 10\text{ V}$ $f = 1\text{ MHz}$		4		pF
$C_{EBO}$	Emitter-Base Capacitance	$I_C = 0$ $V_{EB} = 0.5\text{ V}$ $f = 1\text{ MHz}$		18		pF
NF	Noise Figure	$V_{CE} = 5\text{ V}$ $I_C = 0.1\text{ mA}$ $f = 10\text{ Hz}$ $f_0 = 15.7\text{ KHz}$ $R_n = 1\text{ k}\Omega$		5		dB

#### Electrical Characteristics $T_a = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Test Condition	Min.	Max.	Units
$BV_{CBO}$	Collector-Base Breakdown Voltage	$I_C = 100\text{ }\mu\text{A}$ , $I_E = 0$	30		V
$BV_{CEO}$	Collector-Emitter Breakdown Voltage	$I_C = 1\text{ mA}$ , $I_B = 0$	25		V
$BV_{EBO}$	Emitter-Base Breakdown Voltage	$I_E = 10\text{ }\mu\text{A}$ , $I_C = 0$	3.0		V
$I_{CBO}$	Collector Cut-off Current	$V_{CB} = 25\text{ V}$ , $I_E = 0$		100	nA
$I_{EBO}$	Emitter Cut-off Current	$V_{EB} = 2\text{ V}$ , $I_C = 0$		100	nA
$h_{FE}$	DC Current Gain	$V_{CE} = 10\text{ V}$ , $I_C = 4\text{ mA}$	60		
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_C = 4\text{ mA}$ , $I_B = 0.4\text{ mA}$		0.5	V
$V_{BE(on)}$	Base-Emitter On Voltage	$V_{CE} = 10\text{ V}$ , $I_C = 4\text{ mA}$		0.95	V
$f_T$	Current Gain Bandwidth Product	$V_{CE} = 10\text{ V}$ , $I_C = 4\text{ mA}$ , $f = 100\text{ MHz}$	650		MHz
$C_{ob}$	Output Capacitance	$V_{CB} = 10\text{ V}$ , $I_E = 0$ , $f = 1\text{ MHz}$		0.7	pF
$C_{rb}$	Collector Base Feedback Capacitance	$V_{CB} = 10\text{ V}$ , $I_E = 0$ , $f = 1\text{ MHz}$	0.35	0.65	pF

2N3904

0.31 €

“

Transition frequency is a measure of the high-frequency operating characteristics of a **transistor**, usually symbolized as  $f_T$

“


KSP10

0.27 €


In the 10 kHz-oscillator design, what is the reason to leave out the R1 resistance when building the circuit?

Resistor R1 represents the losses in the real inductor and needs to be taken into account in the simulations.

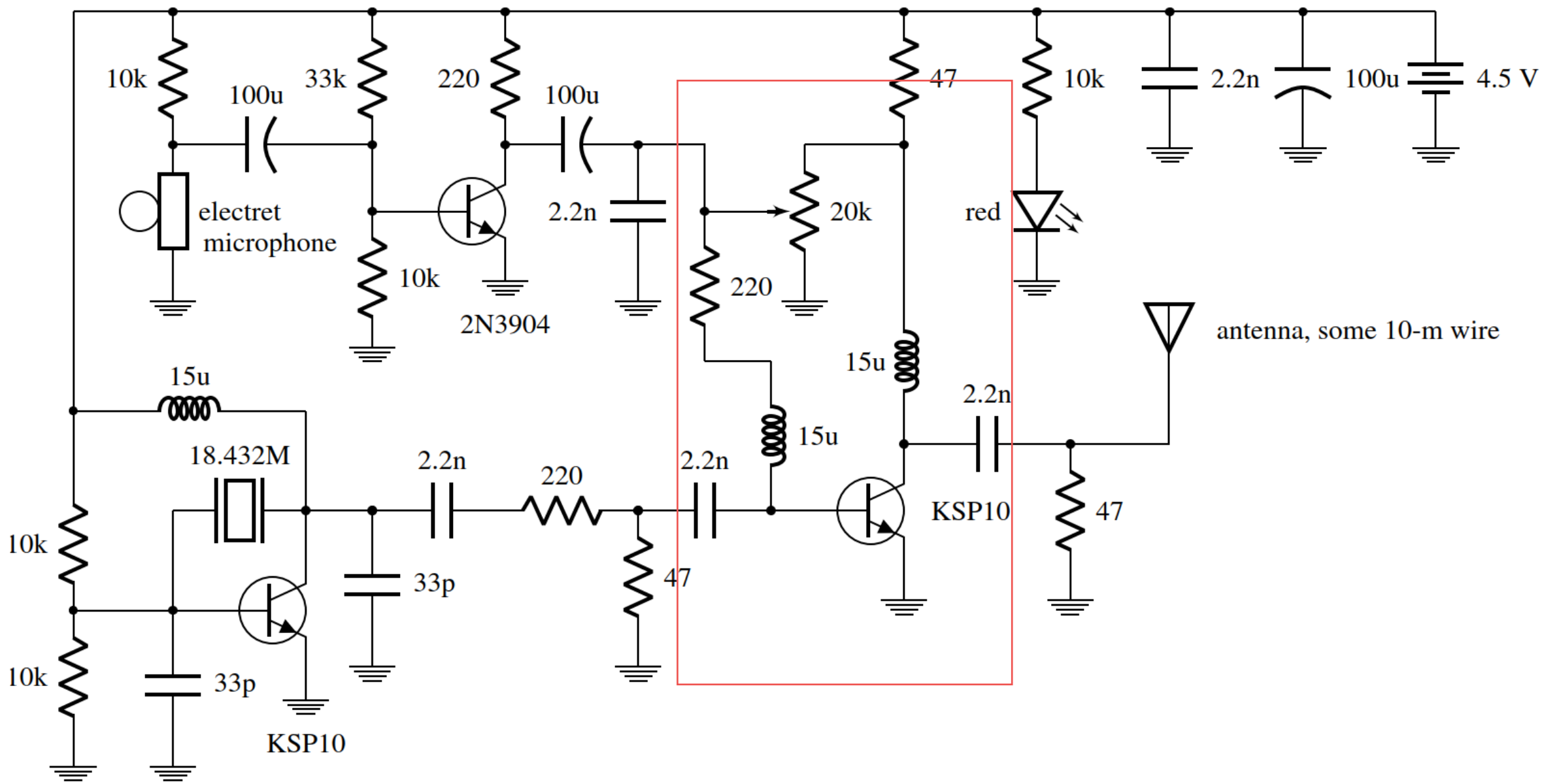Some of you changed the value of R1 closer to the measured in wk2, => simulations and measurements matched better.



# AM biasing

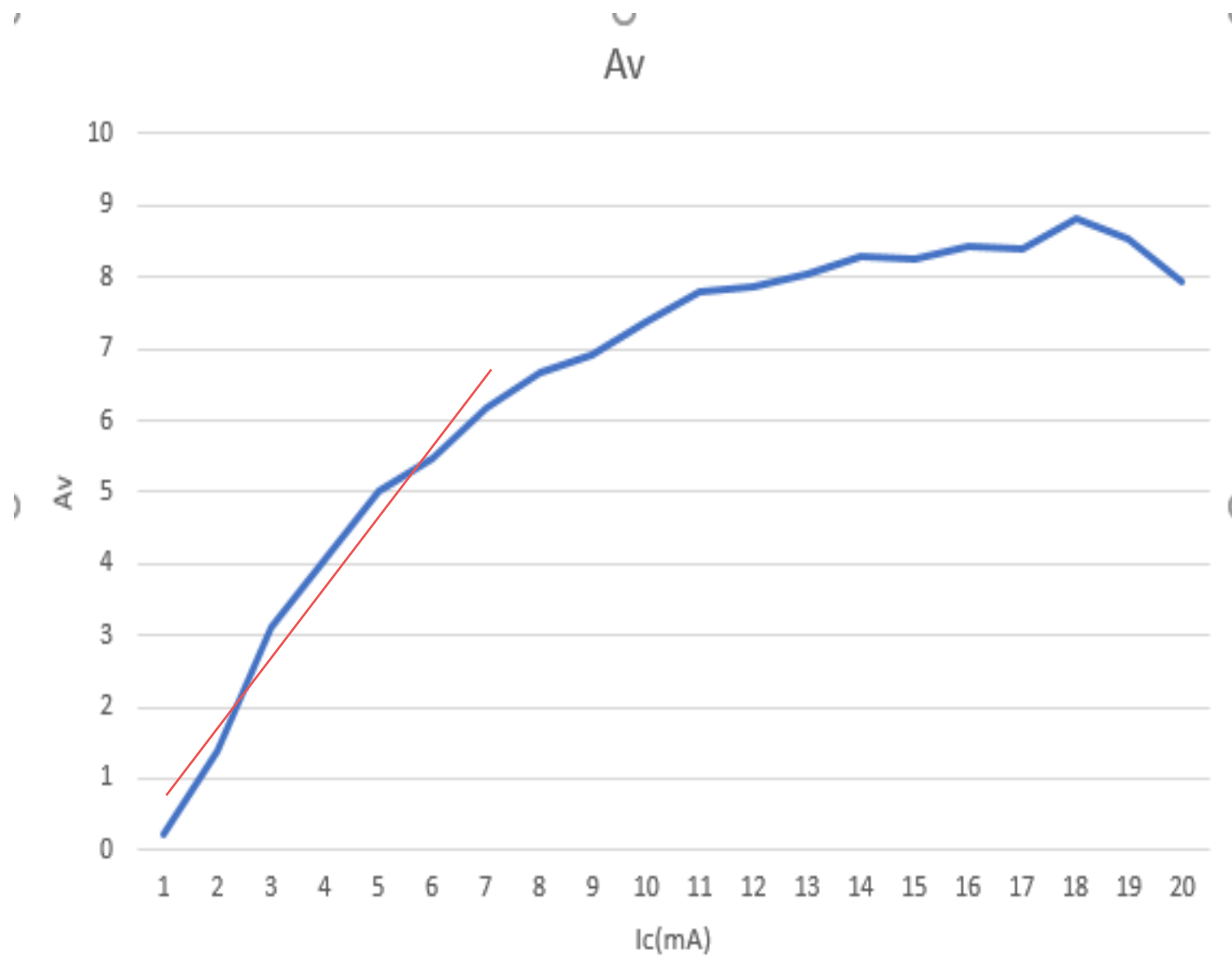




# Oscillator, phase shifter design

Tampere University
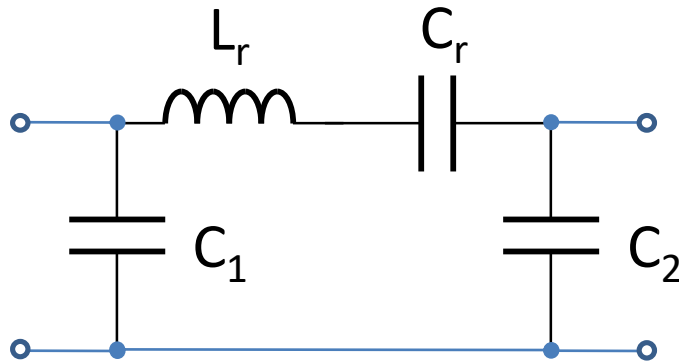
# Oscillator


- How to find the best  $C_1$ ,  $C_2$ ,  $C_r$  and  $L_r$ ?



LC phase shifter for an oscillator
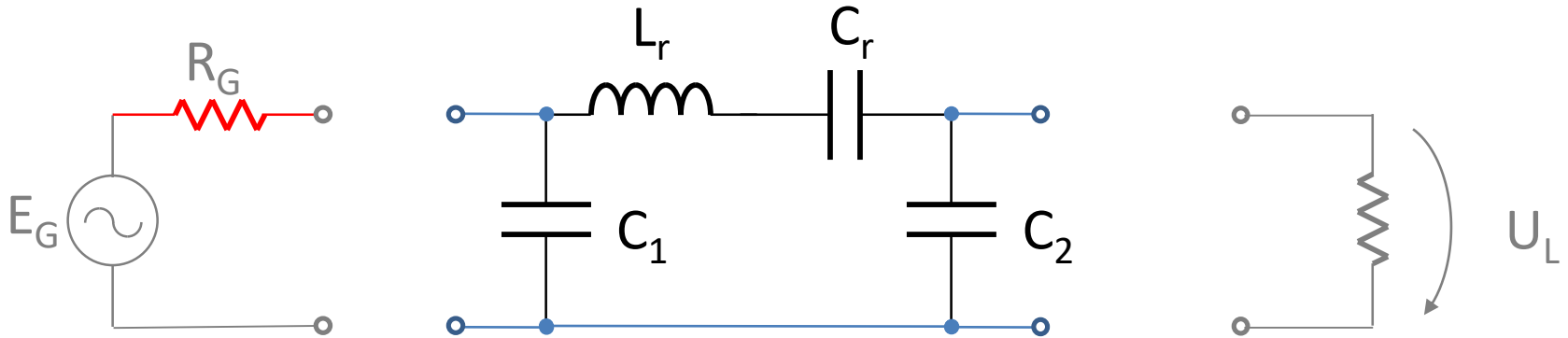
# Oscillator


- How to find the best  $C_1$ ,  $C_2$ ,  $C_r$  and  $L_r$ ?




- In the oscillator application, the phase shifter should provide
  - bandpass response around  $f_0$ 
    - the pass band should be narrow
  - 180-degree phase shift (between  $E_g$  and  $U_L$ ) at  $f_0$ 
    - phase response curve should be steep around  $f_0$ .

# Oscillator


amplitude response  $\text{mag}(2UL/EG)$

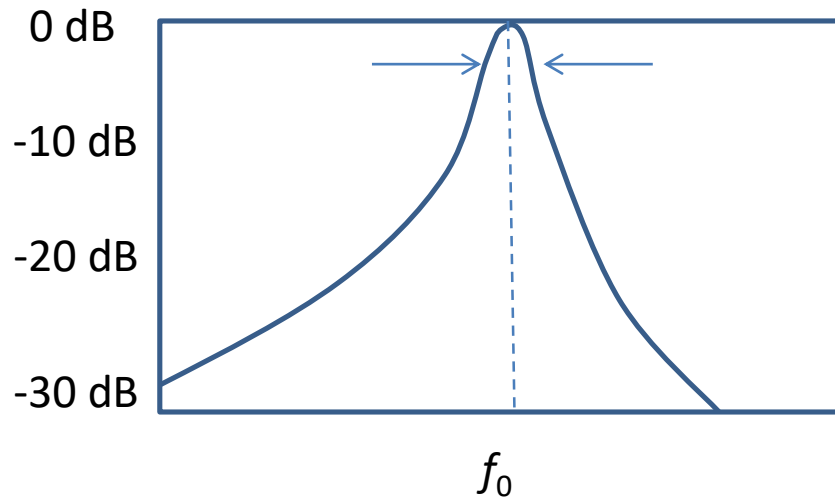

phase response  $\text{ang}(2UL/EG)$

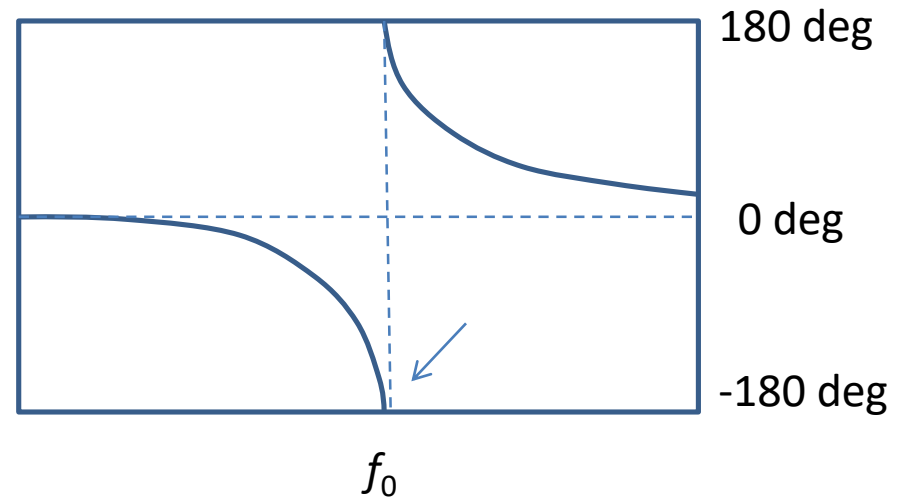


# Oscillator

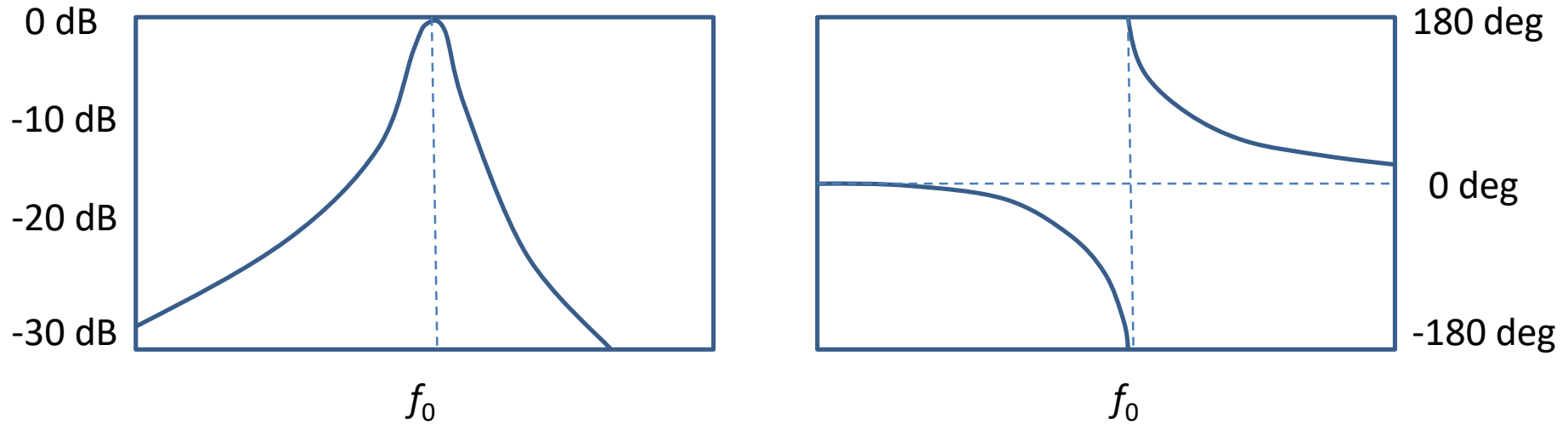

- For narrow-band amplitude response and steep phase response, make:
  1. The LC circuit store a high amount of energy.
  2. Minimum dissipation in all the resistors involved...

# Oscillator

- Resistors involved?

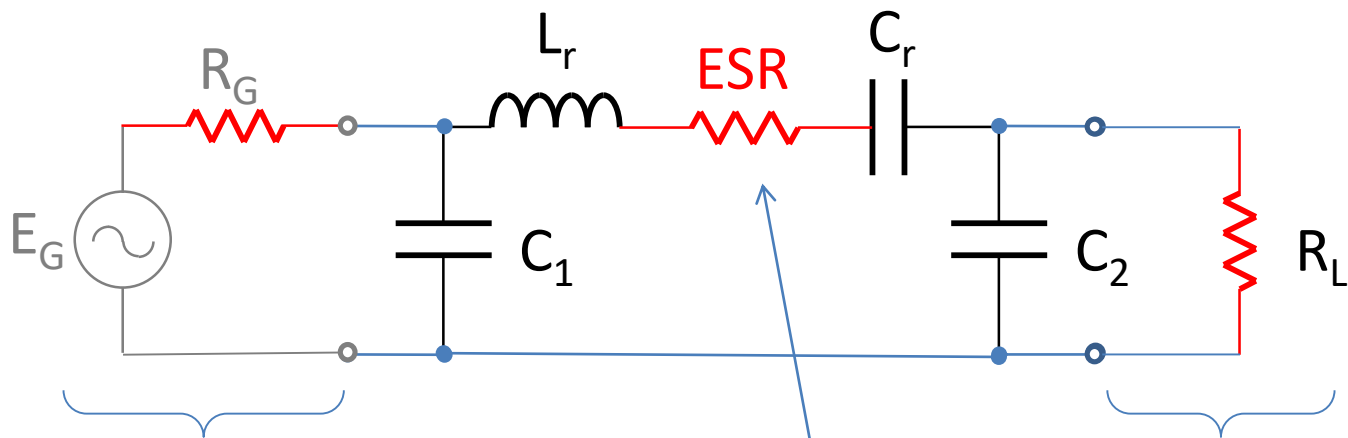


In the oscillator application,  
this is the model of the  
transistor output,

... and this is the model of  
the transistor *input*.

... and this is the equivalent  
series resistance of the inductor  $L_r$   
(and capacitor  $C_r$ , although that is  
usually having less losses).


# Oscillator

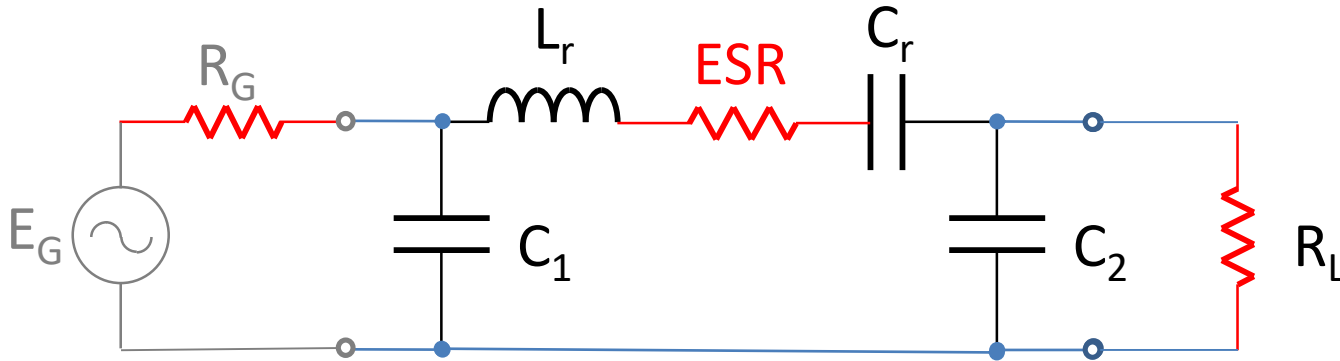


So, how do you mitigate the "Q-spoiling effect" of these resistors?

1. You can bypass (to large degree)  $R_G$  and  $R_L$  by choosing **large  $C_1$  and  $C_2$** 
  - They should be large but, of course,  $C_1$  and  $C_2$  should not *completely* short the signal to ground!
2. You allow large energy storage by choosing **large  $L_r$** 
  - Consequenctly: you need **low  $C_r$**  to maintain  $f_0 \approx 1/(2\pi \cdot \text{sqrt}(L_r C_r))$

# Oscillator

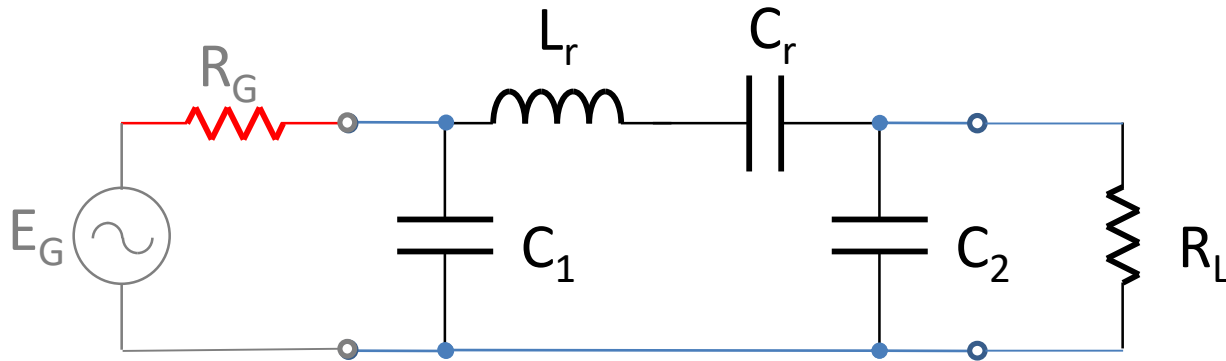


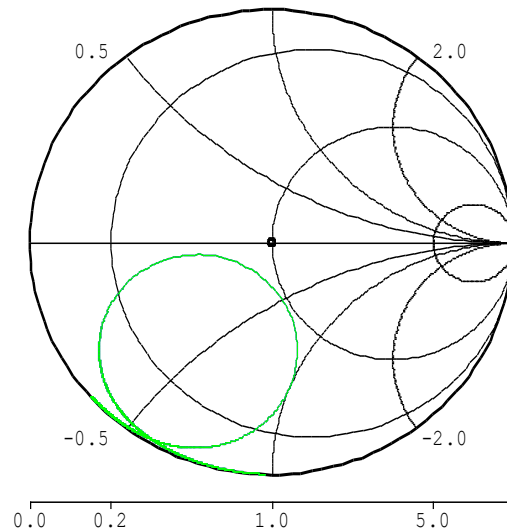$R_g = 50 \, \Omega$   
 $R_L = 50 \, \Omega$   
 $L_r = 3 \mu\text{H}$   
 $Q = 100$   
 $(\text{ESR} = 3.7 \, \Omega)$   
 $C_r = 27 \text{ pF}$   
 $C_1 = 330 \text{ pF}$   
 $C_2 = 330 \text{ pF}$



$S(1,1)$  —

$S(2,2)$  —

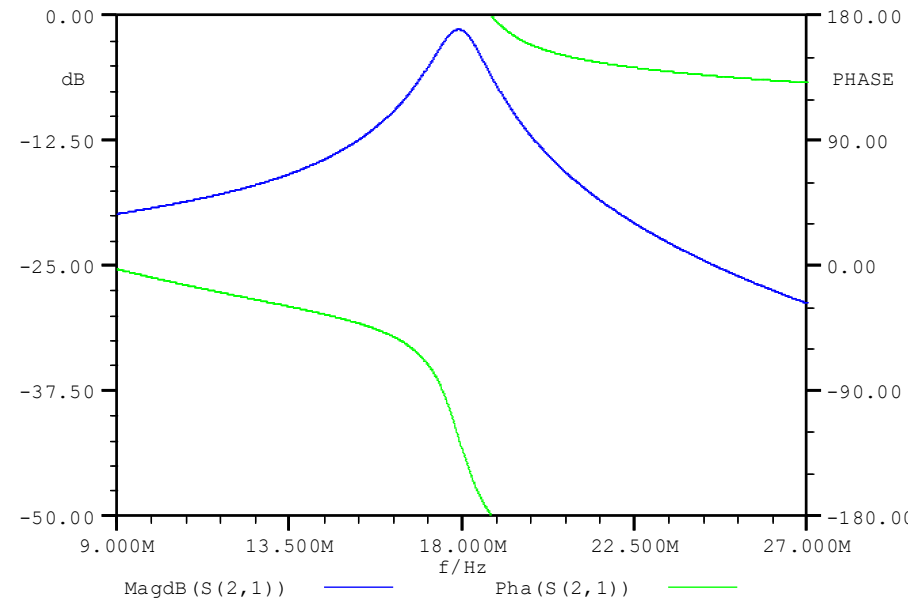

MagnB (S (2,1)) —

Pha (S (2,1)) —



## Scaling up in frequency

When scaling the component values from  $f_1$  to  $f_2$  in a frequency selective circuits we can use criteria that the *impedance* of a reactive component must stay same

$$Z_{f_1} = Z_{f_2}.$$

We obtain “good” initial values for components; in conclusion,

When frequency changes  
 $\Rightarrow$  Component values must change!

## Example: Phase shifter scaling

Consider as an example scaling the 10 kHz phase shifter to work at 18 MHz. We obtain “good” initial values for components. Identify the reactive components in the 10 kHz phase shifter and gather the information to the table below.

Component	@ 10 kHz	@ 18 MHz	E12-value @ 18 MHz
$C_1$ & $C_2$	<b>470 nF</b>	260 pF	270 pF
$C_r$	<b>27 nF</b>	15 pF	15 pF
$L_r$	<b>10 mH</b>	5.5 $\mu$ H	5.6 $\mu$ H
DC block	<b>22 <math>\mu</math>F</b>	12.2 nF	12 nF
RF choke	27 mH	<b>15 <math>\mu</math>H</b>	–

Table 1: Example: scaling up in frequency


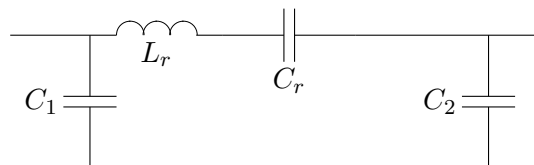


Figure 1: Phase shifter circuit

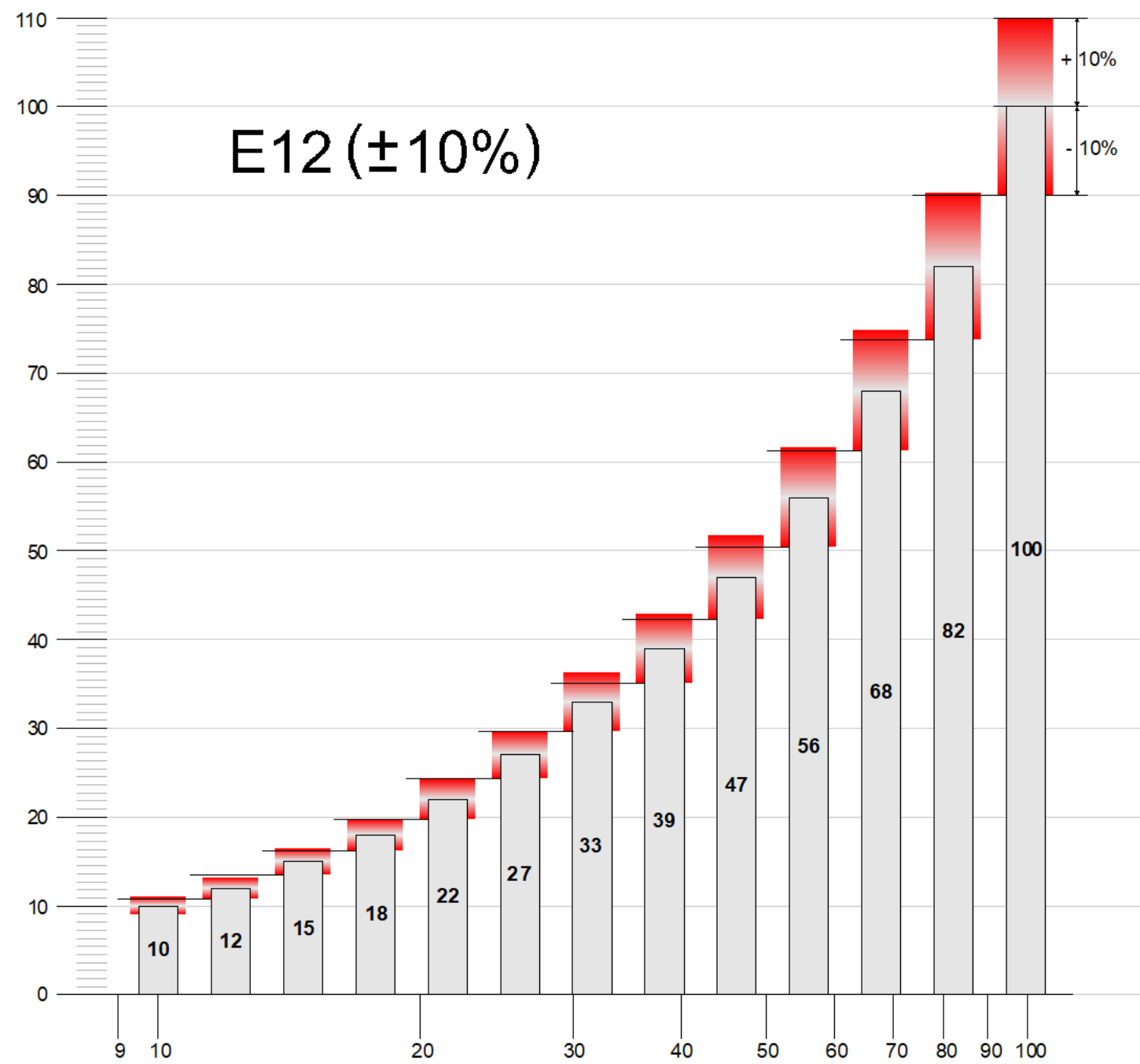

Homework:

Watch an interesting video about oscilloscope probes

[Basic 1X and 10X Oscilloscope Probe tutorial](#)