

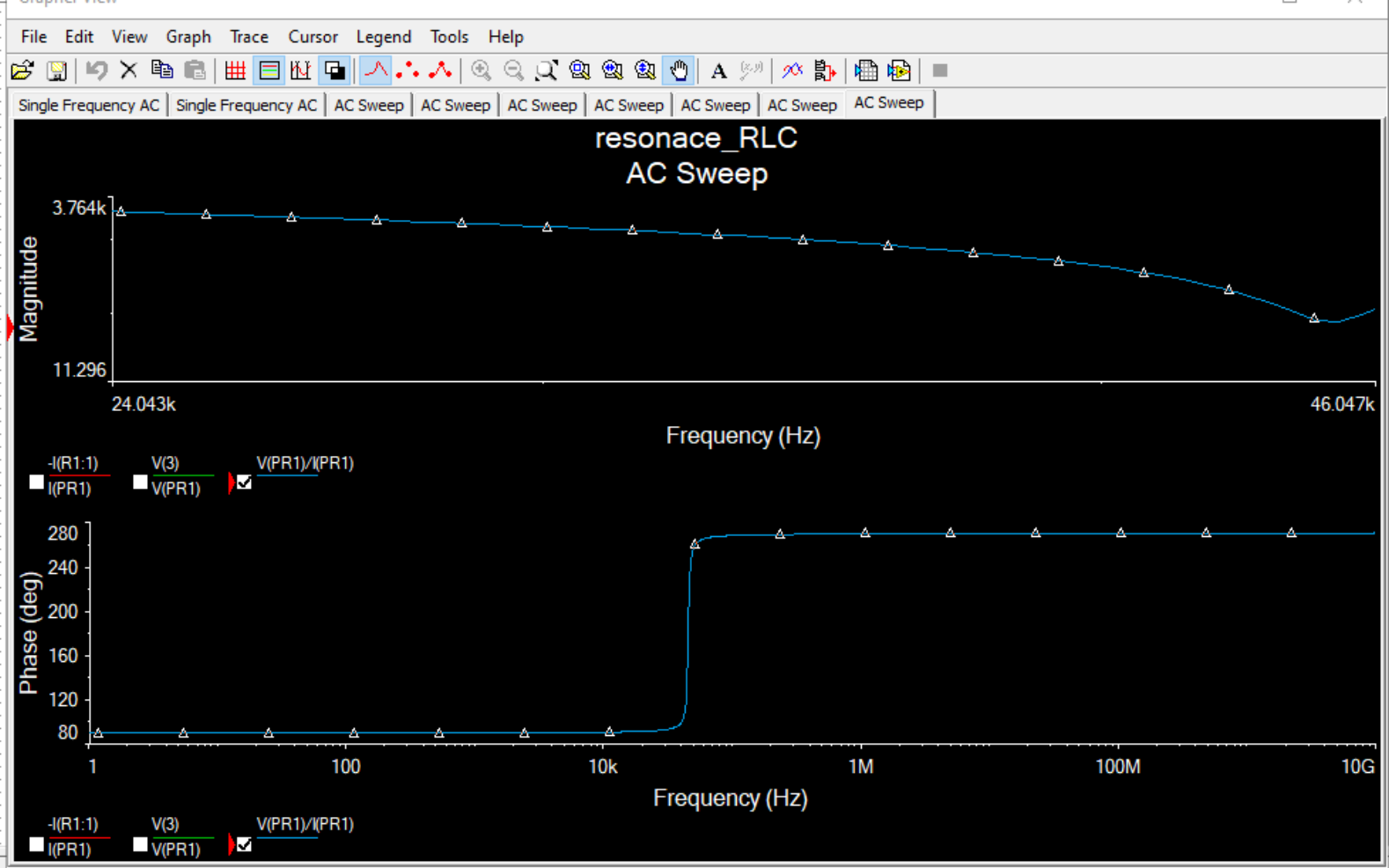


Selected Diagram: AC Sweep

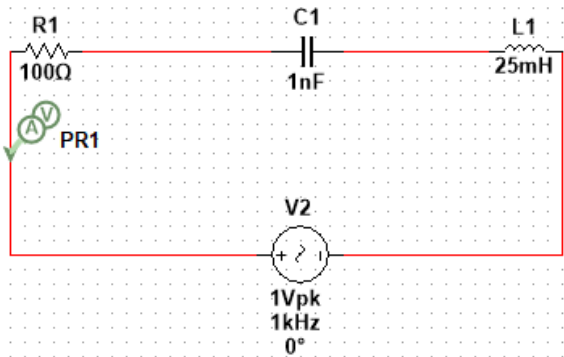

RLC - Resonance.

1/

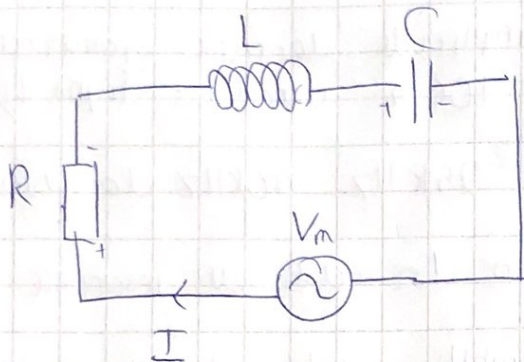

Since ^{Resonance} V_s in frequency f_R appears when the inductive reactance (Z_L) of inductor equal to capacitive reactance (Z_C) of capacitor. Thus we have

$$Z_L = Z_C \Rightarrow 2\pi f_R L = \frac{1}{2\pi f_R C}$$

$$\Rightarrow 4\pi^2 f_R^2 = \frac{1}{LC}$$

$$\Rightarrow f_R^2 = \frac{1}{4\pi^2 LC} \Rightarrow \boxed{f_R = \frac{1}{2\pi\sqrt{LC}}}$$

2/ Since f_R ^{above} equation does not depend on R , in both (a) & (b)

$$\text{We have } f_R = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(25 \cdot 10^{-3})(1 \cdot 10^{-9})}} \approx 31831 \text{ Hz} \\ = 32 \text{ kHz}$$

3/ (a) the two plots represent the amplitude & phase angle of the total impedance Z . Since Z is complex number, it can be presented in polar form, which consisting amplitude & phase angle in frequency domain

(b) In case of 1Ω the amplitude decrease dramatically at near 40kHz while 100Ω it reduce slightly.

Both are considered in $85\text{kHz} - 40\text{kHz}$ domain

(c) In ~~freq~~ phase angle in 1Ω case at resonance frequency, it increase straightly while change in 100Ω is slightly a bit