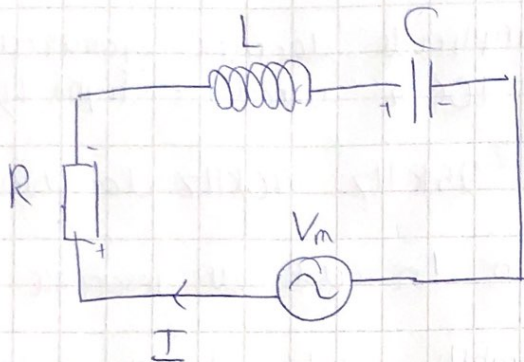


## RLC - Resonance.

1/



Since <sup>Resonance</sup>  $V_s$  in frequency  $f_R$  appears when the inductive reactance ( $Z_L$ ) of inductor equal to capacitive reactance ( $Z_C$ ) of capacitor. Thus we have

$$Z_L = Z_C \Rightarrow 2\pi f_R L = \frac{1}{2\pi f_R C}$$

$$\Rightarrow 4\pi^2 f_R^2 = \frac{1}{LC}$$

$$\Rightarrow f_R^2 = \frac{1}{4\pi^2 LC} \Rightarrow \boxed{f_R = \frac{1}{2\pi\sqrt{LC}}}$$

2/ Since  $f_R$  <sup>above</sup> equation does not depend on  $R$ , in both (a) & (b)

$$\text{We have } f_R = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(25 \cdot 10^{-3})(1 \cdot 10^{-9})}} \approx 31831 \text{ Hz} \\ = 32 \text{ kHz}$$

3/ (a) the two plots represent the amplitude & phase angle of the total impedance  $Z$ . Since  $Z$  is complex number, it can be presented in polar form, which consisting amplitude & phase angle in frequency domain

(b) In case of  $1\Omega$  the amplitude decrease dramatically at near  $40\text{kHz}$  while  $100\Omega$  it reduce slightly.

Both are considered in  $85\text{kHz} - 40\text{kHz}$  domain

(c) In ~~freq~~ phase angle in  $1\Omega$  case at resonance frequency, it increase straightly while change in  $100\Omega$  is slightly a bit