

Lets study a series RLC resonance circuit. You first analyze it with paper-and-pen. Then you use AC analysis in Multisim to simulate the case.

1. Draw a series RLC resonance circuit. Find expression for the resonance frequency of the circuit.

---

Series RLC: The total impedance  $Z_S = R + j\omega L - j\frac{1}{\omega C}$ .

Resonance when for  $\omega_r$  holds  $\text{Imag}(Z_S(\omega_r)) = 0 \Rightarrow \left(\omega_r L - \frac{1}{\omega_r C}\right) = 0$

which gives  $\omega_r = \frac{1}{\sqrt{LC}}$  and  $Z_S(\omega_r) = R$ .

---

2. Find the resonance frequency when  $L = 25 \text{ mH}$ ,  $C = 1 \text{ nF}$ , and  $R$  is

- (a)  $1 \text{ } \Omega$  and

- (b)  $100 \text{ } \Omega$ .

---

$R = 1 \text{ } \Omega$  and  $R = 100 \text{ } \Omega \Rightarrow \omega_r = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{25 \text{ mH } 1 \text{ nF}}} = 200000 \text{ rad}$

such that  $f_r = 31.831 \text{ kHz}$ .

---

3. Simulate the series resonance circuit using Multisim, look at the impedance of the circuit over frequency range  $25 \text{ kHz} - 40 \text{ kHz}$ .

In the simulations use

- “Sweep Type” as “Decade”
- “Number of points per decade” (at least) 200
- “Vertical scale” as logarithmic

- (a) Explain first briefly how to relate the two plots that appear in the screen.

- (b) Compare the amplitude plots for the these two cases. You are likely to find useful “Zoom in Area”-command.

- (c) Which differences you notice between the two cases?

Following links are likely useful for you in question 3:

- <http://digital.ni.com/public.nsf/allkb/9F8D30235DE3EC0186257592006B23A2>
- <http://www.ni.com/tutorial/12690/en/>.

# Simulation result with R=100 ohms

